

# Logic Circuit

Problem ID: a02p07logiccircuit

Here is a simple logic circuit that has 3 inputs,  $A$ ,  $B$ , and  $C$ , and 1 output  $D$ .

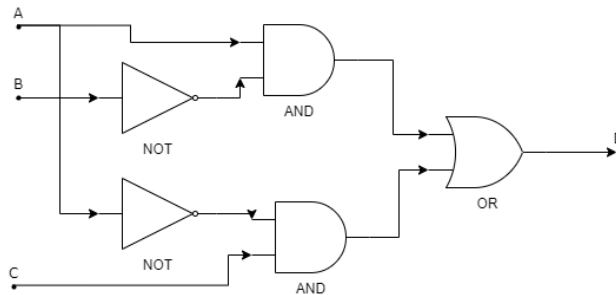


Figure 1: The logic circuit

The circuit contains three types of logic gates:

- A NOT gate takes one input  $x$ , and outputs 1 if  $x = 0$ , but 0 otherwise.
- An AND gate takes two inputs  $x$  and  $y$ , and outputs 1 if  $x = y = 1$ , but 0 otherwise.
- An OR gate takes two inputs  $x$  and  $y$ , and outputs 0 if  $x = y = 0$ , but 1 otherwise.

Write a program that is equivalent to the logic circuit above.

## Input

Input consists of three lines. The first line contains the integer  $A$ , where  $A$  is either 0 or 1. The second line contains the integer  $B$ , where  $B$  is either 0 or 1. The third line contains the integer  $C$ , where  $C$  is either 0 or 1.

## Output

Output the value of  $D$ , which is either 0 or 1.

| Sample Input 1 | Sample Output 1 |
|----------------|-----------------|
| 0<br>0<br>0    | 0               |
| Sample Input 2 | Sample Output 2 |
| 0<br>0<br>1    | 1               |
| Sample Input 3 | Sample Output 3 |
| 1<br>1<br>1    | 0               |
| Sample Input 4 | Sample Output 4 |
| 1<br>0<br>0    | 1               |

**Sample Input 5**

1  
1  
0

**Sample Output 5**

0